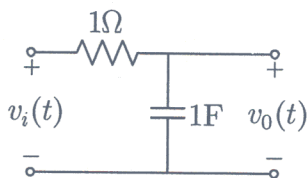


DRUGI KOLOKVIJUM IZ TEORIJE ELEKTRIČNIH KOLA – A


1(2p). Primjenom Laplasove transformacije odrediti odziv  $v(t)$  ako je dinamika nekog električnog kola opisana sledećom relacijom  $\frac{dv(t)}{dt} + 5v(t) + 6 \int_0^t v(\tau)d\tau = h(t)$  i ako je  $v(0) = 2$ .

2(3p).



Ulazni signal u kolu prikazanom na slici je jednak  $v_i(t) = 10e^{-5t}h(t)$  V. Odrediti ukupnu energiju izlaznog signala  $v_0(t)$  razvijenu na otporniku od  $1\Omega$ .

3(4p).

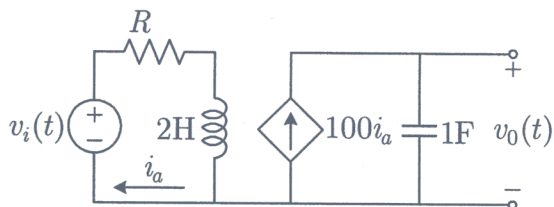


Funkcija prenosa kola prikazanog na slici jednaka je:

$$H(j\omega) = \frac{V_0(j\omega)}{V_i(j\omega)} = \frac{5}{j\omega(1 + j\frac{\omega}{10})}$$

Odrediti vrijednost otpornosti  $R$  u prikazanom kolu u  $\Omega$ .


4(6p).

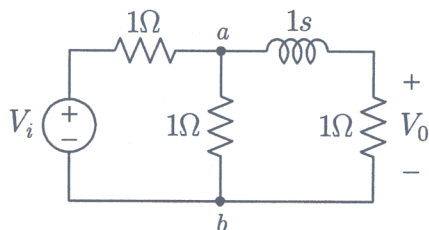

Za kolo prikazano u  $s$ -domenu odrediti:

- Funkciju prenosa kola  $H(s) = V_0(s)/V_i(s)$  (1.5p).
- Impulsni odziv kola (1.5p).
- Jedinični (step) odziv (1.5p).
- Odziv kada je  $v_i(t) = 8 \cos 2t$  V (1.5p)

5(5p).

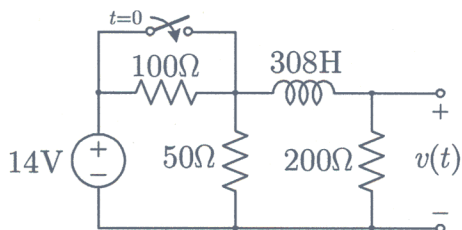

Odziv kola prikazanog na slici je jednak  $v(t) = A + Be^{-at}$  V za  $t > 0$ . Odrediti vrijednost konstante  $B$  u izrazu za izlazni napon u V.

**NAPOMENA:** Za izradu kolokvijuma student dobija tri lista i na kraju ispita moraju biti svi vraćeni. Dozvoljena je upotreba samo tabela i šema koje su dobijene na računskim vježbama. Na prvoj stranici napisati sledeće: DRUGI KOLOKVIJUM IZ TEORIJE ELEKTRIČNIH KOLA, ime i prezime i broj indeksa. Rad nastaviti na prvoj slobodnoj stranici. **OBAVEZNO ISKLJUČITI MOBILNE TELEFONE.**

Ispit traje 90 minuta.

PREDMETNI NASTAVNIK

GRUPA (A)

#1  $\frac{dv(t)}{dt} + 5v(t) + 6 \int_0^t v(\tau) d\tau = f(t)$  ;  $v(0) = 2$

PRIMENOM LAPLASSOVE TRANSFORMACIJE NA GORNJU RELACIJU DOBIJAMO:


$[sV(s) - v(0)] + 5V(s) + \frac{6}{s} V(s) = \frac{1}{s} \Rightarrow V(s)(s^2 + 5s + 6) = 1 + 2s$

$V(s) = \frac{2s+1}{s^2+5s+6} = \frac{A}{s+2} + \frac{B}{s+3} \Rightarrow A = -3 ; B = 5$

$v(t) = \mathcal{L}^{-1}\{V(s)\} = \mathcal{L}^{-1}\left\{\frac{-3}{s+2} + \frac{5}{s+3}\right\} \Rightarrow v(t) = (-3e^{-2t} + 5e^{-3t})$
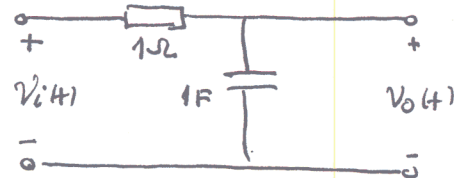
#2  $V_i(j\omega) = \frac{10}{j\omega+5}$  ;  $H(j\omega) = \frac{1}{1+\frac{1}{j\omega}} = \frac{1}{1+j\omega}$

$V_o(j\omega) = H(j\omega) V_i(j\omega) = \frac{10}{(1+j\omega)(5+j\omega)}$




$|V_o(j\omega)|^2 = \frac{100}{(1+\omega^2)(25+\omega^2)} = \frac{100}{24} \left[ \frac{1}{1+\omega^2} - \frac{1}{25+\omega^2} \right] = \frac{25}{6} \left[ \frac{1}{1+\omega^2} - \frac{1}{25+\omega^2} \right]$

$W = \frac{1}{2\pi} \int_{-\infty}^{\infty} |V_o(j\omega)|^2 d\omega = \frac{25}{12\pi} \left\{ \int_{-\infty}^{\infty} \frac{d\omega}{1+\omega^2} - \int_{-\infty}^{\infty} \frac{25}{\omega^2+25} d\omega \right\}$

$W = \frac{25}{12\pi} \left\{ \arctan(\omega) \Big|_{-\infty}^{\infty} - \frac{1}{5} \arctan\left(\frac{\omega}{5}\right) \Big|_{-\infty}^{\infty} \right\} = \frac{25}{12\pi} \left[ \pi - \frac{\pi}{5} \right] = \frac{5}{3} \text{ J}$

#3 (\*)  $H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{5}{j\omega(1+j\frac{\omega}{10})}$

SA SLIKOM:

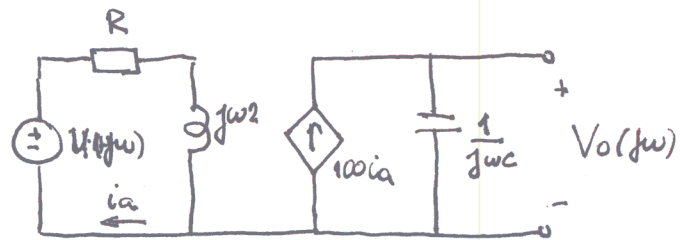

$V_o(j\omega) = \frac{1}{j\omega C} 100 I_a(j\omega)$

$= \frac{1}{j\omega} 100 I_a(j\omega)$

$I_a(j\omega) = \frac{V_i(j\omega)}{R+2j\omega}$


$\Rightarrow V_o(j\omega) = \frac{1}{j\omega} 100 \frac{V_i(j\omega)}{R+2j\omega}$   
 (\*\*\*)  $\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{100}{j\omega(R+2j\omega)} = \frac{5}{j\omega(\frac{R}{20} + j\frac{\omega}{10})}$

UPOREĐUJUĆI (\*) I (\*\*\*) VIDIMO DA JE

$R = 20 \Omega$

#4 a) PRIMENOM DJELOVITELJA NAPONA DOBIJAMO:

$V_o(s) = \frac{1}{s+1} V_{ab}(s)$

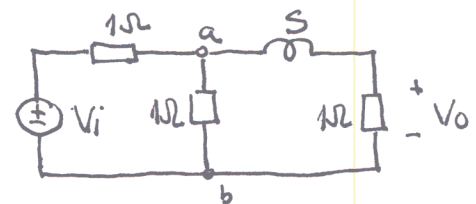

$V_{ab}(s) = \frac{1 \parallel (s+1)}{1 + 1 \parallel (s+1)} V_i(s) = \frac{\frac{s+1}{s+2}}{1 + \frac{s+1}{s+2}} V_i(s) \Rightarrow V_{ab}(s) = \frac{s+1}{2s+3} V_i(s)$

$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{2s+3}$

$$\#4 \text{ b) } H(s) = \frac{1}{2s+3} = \frac{1}{2} \frac{1}{s+\frac{3}{2}}$$

IMPULSNI ODZIV

$$g(t) = \mathcal{L}^{-1}\{H(s)\} \Rightarrow g(t) = \frac{1}{2} e^{-t\frac{3}{2}} \chi(t)$$

c) Kada je  $v_i(t) = \chi(t)$ ,  $V_i(s) = \frac{1}{s}$  pa je STEP odziv

$$V_o(s) = H(s) V_i(s) = \frac{1}{2s(s+\frac{3}{2})} = \frac{A}{s} + \frac{B}{s+\frac{3}{2}} = \frac{1}{3} \left( \frac{1}{s} + \frac{1}{s+\frac{3}{2}} \right) \quad \begin{matrix} A = \frac{1}{3} \\ B = -\frac{1}{3} \end{matrix}$$

$$V_o(t) = \mathcal{L}^{-1}\{V_o(s)\} \Rightarrow V_o(t) = \frac{1}{3} (1 - e^{-\frac{3t}{2}}) \chi(t) \text{ V}$$

$$\text{d) } v_i(t) = 8 \cos 2t \quad v_i(s) = \frac{8s}{s^2+4}$$


$$V_o(s) = H(s) V_i(s) = \frac{4s}{(s+\frac{3}{2})(s^2+4)} = \frac{A}{s+\frac{3}{2}} + \frac{Bs+C}{s^2+4} \quad \left. \begin{matrix} A = -\frac{24}{25} \\ B = +\frac{20}{25} \\ C = +\frac{16}{25} \end{matrix} \right\}$$

$$V_o(s) = \frac{-\frac{24}{25}}{s+\frac{3}{2}} + \frac{20}{25} \frac{s}{s^2+4} + \frac{16}{25} \frac{2}{s^2+4}$$

$$V_o(t) = \mathcal{L}^{-1}\{V_o(s)\} \Rightarrow V_o(t) = \frac{24}{25} (-e^{-\frac{3t}{2}} + \cos 2t + \frac{4}{3} \sin 2t) \chi(t) \text{ V}$$
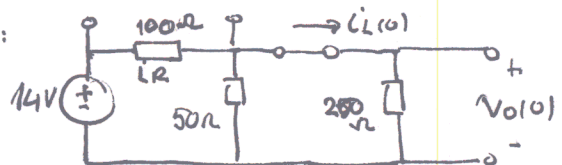
#5. KOLO U TRENUTKU  $t=0$  JE OBLIKA:

$$i_R = \frac{14}{100 + \frac{50 \cdot 200}{250}} = \frac{14}{140} = 0,1 \text{ A}$$



RAZDJELENIK STRUJE:

$$i_{L(0)} = \frac{50}{50+200} \cdot 0,1 \Rightarrow i_{L(0)} = 0,02 \text{ A}$$

$$L i_{L(0)} = 308(0,02) = 6,16 \text{ V}$$

KOLO U S-DOMENU (NAKON ZATVARANJA PREKIDACA)

$$50 [i_1(s) - i_2(s)] = \frac{14}{s}$$

$$(308s + 200) i_2(s) - L i_{L(0)} - 50 [i_1(s) - i_2(s)] = \frac{14}{s}$$

$$(308s + 200) i_2(s) = \frac{14}{s} + L i_{L(0)} / 308$$


$$i_2(s) = \frac{0,045 + 0,025}{s(s+0,64)}$$

$$V_2(s) = 200 \cdot i_2(s) = \frac{9 + 4s}{s(s+0,64)} = \frac{A}{s} + \frac{B}{s+0,64}$$

$$A = 14, \quad B = -10$$

$$V_2(t) = \mathcal{L}^{-1}\{V_2(s)\} = 14 - 10 e^{-0,64t} \text{ V}$$

$$\Rightarrow B = -10 \text{ V}$$

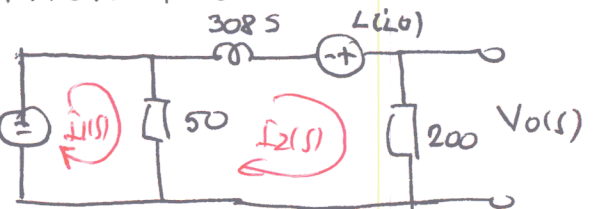

# ELEKTROTEHNIČKI FAKULTET

## AKADEMSKE OSNOVNE STUDIJE ELEKTROTEHNIKE


STUDIJSKI PROGRAMI: ELEKTRONIKA, RAČUNARI, TELEKOMUNIKACIJE, ENERGETIKA I AUTOMATIKA

23. 11. 2006. godine

### DRUGI KOLOKVIJUM IZ TEORIJE ELEKTRIČNIH KOLA – B


1(2p). Primjenom Laplasove transformacije odrediti odziv  $v(t)$  ako je dinamika nekog električnog kola opisana sledećom relacijom  $\frac{dv(t)}{dt} + 3v(t) + 2 \int_0^t v(\tau) d\tau = 2e^{-3t}$  i ako je  $v(0) = 0$ .

2(3p).

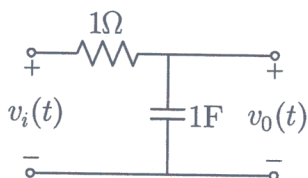

Ulazni signal u kolu prikazanom na slici je jednak  $v_i(t) = 10e^{-5t}h(t)$  V. Odrediti energiju izlaznog signala  $v_0(t)$  razvijenu na otporniku od  $1\Omega$  u frekventnom opsegu  $2 < \omega < 4$  rad/s.

3(4p).

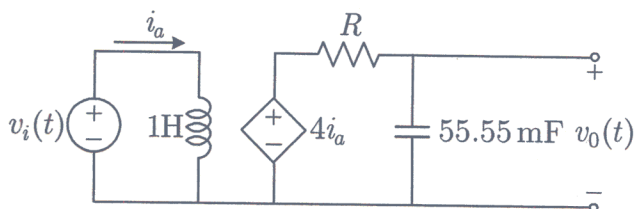


Funkcija prenosa kola prikazanog na slici jednaka je:

$$H(j\omega) = \frac{V_0(j\omega)}{V_i(j\omega)} = \frac{4}{j\omega(1 + j\frac{\omega}{18})}$$

Odrediti vrijednost otpornosti  $R$  u prikazanom kolu u  $\Omega$ .


4(6p).

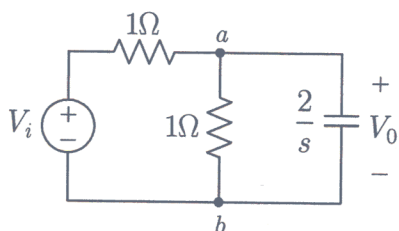

Za kolo prikazano u  $s$ -domenu odrediti:

- Funkciju prenosa kola  $H(s) = V_0(s)/V_i(s)$  (1.5p).
- Impulsni odziv kola (1.5p).
- Jedinični (step) odziv (1.5p).
- Odziv kada je  $v_i(t) = 8 \cos 2t$  V (1.5p).

5(5p).

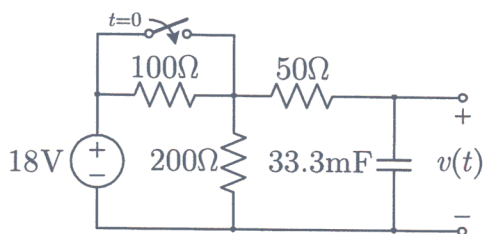

Odziv kola prikazanog na slici je jednak  $v(t) = A + Be^{-at}$  V za  $t > 0$ . Odrediti vrijednost konstante  $B$  u izrazu za izlazni napon u V.

**NAPOMENA:** Za izradu kolokvijuma student dobija tri lista i na kraju ispita moraju biti svi vraćeni. Dozvoljena je upotreba samo tabela i šema koje su dobijene na računskim vježbama. Na prvoj stranici napisati sledeće: **DRUGI KOLOKVIJUM IZ TEORIJE ELEKTRIČNIH KOLA**, ime i prezime i broj indeksa. Rad nastaviti na prvoj slobodnoj stranici. **OBAVEZNO ISKLJUČITI MOBILNE TELEFONE.**

Ispit traje 90 minuta.

PREDMETNI NASTAVNIK



GRUPA (B)

#1  $\frac{dv(t)}{dt} + 3v(t) + 2 \int_0^t v(\tau) d\tau = 2e^{-3t}$  ;  $v(0) = 0$

PRIMJENOM LAPLASSOVE TRANSFORMACIJE DOBIJAMO:

$sV(s) - v(0) + 3V(s) + \frac{2}{s}V(s) = \frac{2}{s+3}$


$[s^2 + 3s + 2]V(s) = \frac{2s}{s+3} \Rightarrow V(s) = \frac{2s}{(s+1)(s+2)(s+3)}$

$V(s) = \frac{A}{s+1} + \frac{B}{s+2} + \frac{C}{s+3} \{ A = -1, B = 4, C = -3 \} = -\frac{1}{s+1} + \frac{4}{s+2} + \frac{3}{s+3}$

$v(t) = \mathcal{L}^{-1}\{V(s)\} = (-e^{-t} + 4e^{-2t} - 3e^{-3t}) \cdot \mathcal{L}^{-1}\{1\}$
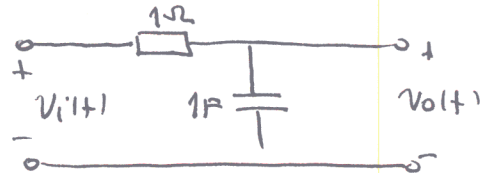
#2  $V_i(j\omega) = \frac{10}{5+j\omega}$  ;  $H(j\omega) = \frac{1}{1+j\omega}$

$V_o(j\omega) = H(j\omega) V_i(j\omega) = \frac{10}{(1+j\omega)(5+j\omega)}$



$|V_o(j\omega)|^2 = \frac{25}{6} \left[ \frac{1}{1+\omega^2} + \frac{1}{25+\omega^2} \right]$


$W = \frac{25}{6\pi} \left[ \int_2^4 \frac{d\omega}{1+\omega^2} - \int_2^4 \frac{d\omega}{25+\omega^2} \right] = \frac{25}{6\pi} \left\{ \arctg(\omega) \Big|_2^4 - \frac{1}{5} \arctg\left(\frac{\omega}{5}\right) \Big|_2^4 \right\}$

$W = \frac{25}{6\pi} \left\{ 1,326 - 1,107 - \frac{(0,675 - 0,381)}{5} \right\} \Rightarrow W = 0,212 \text{ J}$
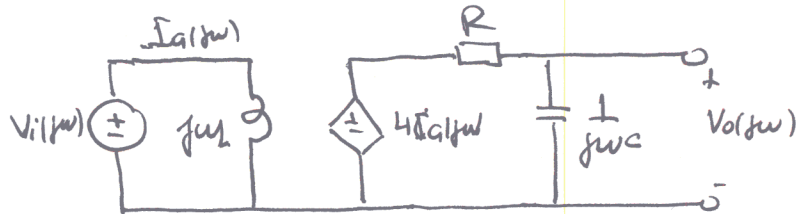
#3  $V_i(j\omega) = I_a(j\omega) \cdot j\omega L$

$I_a(j\omega) = \frac{V_i(j\omega)}{j\omega}$

$4 \frac{V_i(j\omega)}{j\omega} = \frac{1+j\omega RC}{j\omega C}$




$V_o(j\omega) = \frac{1}{j\omega C} \cdot \frac{4C V_i(j\omega)}{1+j\omega RC} \Rightarrow H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{4}{j\omega(1+j\omega RC)}$  (\*)

$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{4}{j\omega(1+j\frac{\omega}{1/R})}$  (\*\*)

17 (\*) i (\*\*)

$\Rightarrow RC = \frac{1}{18} \Rightarrow R = \frac{10^3}{18 \cdot 55 \cdot 55} \Rightarrow R = 1 \Omega$
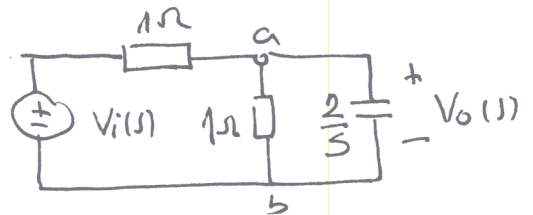
#4 a)  $\frac{V_o(s)}{V_i(s)} = \frac{1 + \frac{2}{3}}{1 + \frac{2}{3} \cdot 11} = \frac{2s}{1 + \frac{2s}{3}} = \frac{2}{s+4}$



$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{2}{s+4}$

b)  $H(s) = \frac{2}{s+4} \Rightarrow$  Impulseni odziv je  $g(t) = \mathcal{L}^{-1}\{H(s)\}$

$g(t) = 2e^{-4t} \mathcal{L}(t)$

$$\#4 c) V_o(s) = H(s) V_i(s) = \frac{2}{s(s+4)} = \frac{A}{s} + \frac{B}{s+4} \quad \left\{ \begin{array}{l} A = \frac{1}{2} \\ B = -\frac{1}{2} \end{array} \right.$$

$$V_o(s) = \frac{1}{2} \left[ \frac{1}{s} - \frac{1}{s+4} \right] \Rightarrow V_o(t) = \mathcal{L}^{-1} \{ V_o(s) \}$$

$$V_o(t) = \frac{1}{2} (1 - e^{-4t}) \cdot 2(4) \text{ V}$$

$$d) V_i(t) = 8 \cos 2t \Rightarrow V_i(s) = \frac{8s}{s^2+4}$$

$$V_o(s) = H(s) V_i(s) = \frac{16s}{(s+4)(s^2+4)} = \frac{A}{s+4} + \frac{Bs+C}{s^2+4}$$

$$\left\{ A = -\frac{16}{5}; B = \frac{16}{5}; C = \frac{16}{5} \right\} \Rightarrow V_o(s) = \frac{16}{5} \left[ -\frac{1}{s+4} + \frac{s+1}{s^2+4} \right]$$

$$V_o(s) = \frac{16}{5} \left[ -\frac{1}{s+4} + \frac{s}{s^2+4} + \frac{1}{2} \frac{2}{s^2+4} \right]$$

$$V_o(t) = \mathcal{L}^{-1} \{ V_o(s) \} = \frac{16}{5} \left[ -e^{-4t} + \cos 2t + \frac{1}{2} \sin 2t \right] \cdot 2(4) \text{ V}$$

#5 KOLO U TREKUTKU  $t=0$  JE OBLIKA:

$$i_R = \frac{18}{100+200} = 0,06 \text{ A}$$

$$V_o(0) = 200 \cdot 0,06 = 12 \text{ V}$$

KOLO U S-DOMENU (NAKON ZATVARANJA PREKIDAČA)

$$\frac{1}{sC} = \frac{1}{s \cdot \frac{100}{3} \cdot 10^{-3}} = \frac{3}{0,1 \cdot s}$$

$$200 [I_1(s) - I_2(s)] = \frac{18}{s}$$

$$\frac{1}{2} \Omega (50 + \frac{3}{0,1 \cdot s}) + \frac{12}{s} - \frac{18}{s} = 0$$

$$I_2(s) (50 + \frac{3}{0,1 \cdot s}) = \frac{6}{s} \Big/ \frac{5}{50} \Rightarrow (s + \frac{3}{5}) I_2(s) = \frac{3}{2s} = 0,2$$

$$I_2(s) = \frac{0,12}{s+0,6}$$

$$V_o(s) = \frac{3}{0,1s} I_2(s) + \frac{12}{s} = \frac{3,6}{s(s+0,6)} + \frac{12}{s}$$

$$V_o(s) = \frac{A}{s} + \frac{B}{s+0,6} + \frac{12}{s} \quad \left\{ \begin{array}{l} A = 6 \\ B = -6 \end{array} \right\} = \frac{18}{s} - \frac{6}{s+0,6}$$

$$V_o(t) = 18 - 6 e^{-0,6t}$$

$$V_o(t) = A + B e^{-at} \Rightarrow B = -6 \text{ V}$$

